
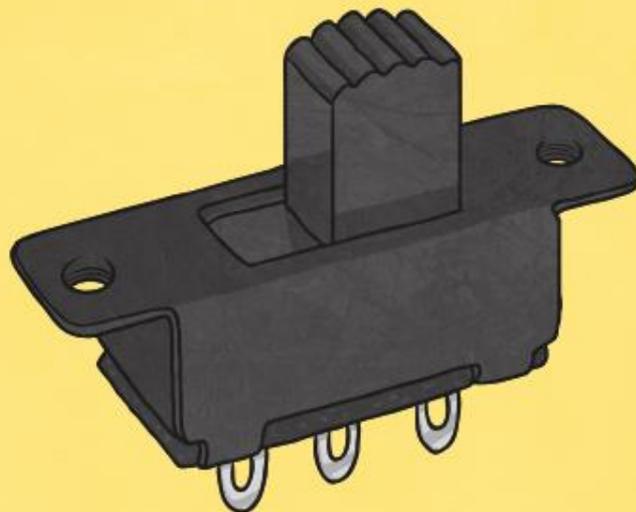


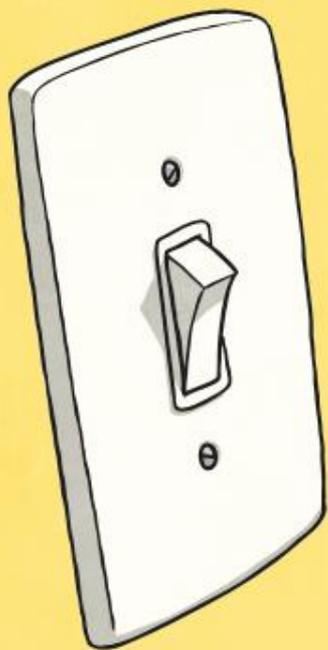

Science

Electricity

Splendid Switches



twinkl

Aim

- I can explain how a switch works and why they are needed.

Success Criteria

- I can explain that a switch turns the electric current on and off.
- I can create a circuit containing a switch.



Parts of a Circuit



crocodile clip





motor

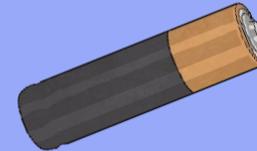
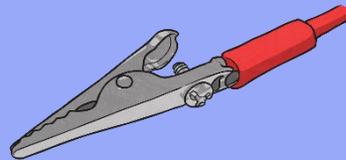


bulb

wires

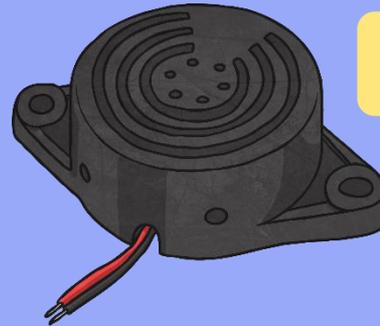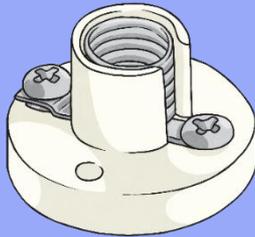

battery (cell)

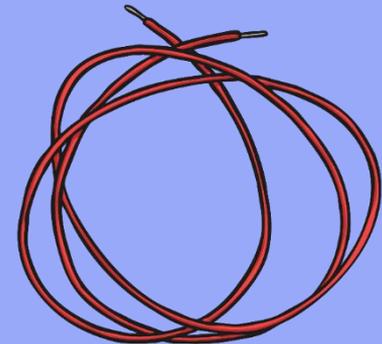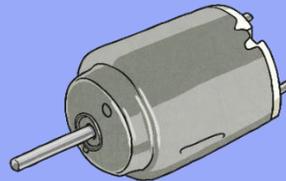

Which cards are new to you? What do those parts do?

Bulbs, Buzzers and Motors



What examples of circuits which include bulbs/buzzers/motors do you know?



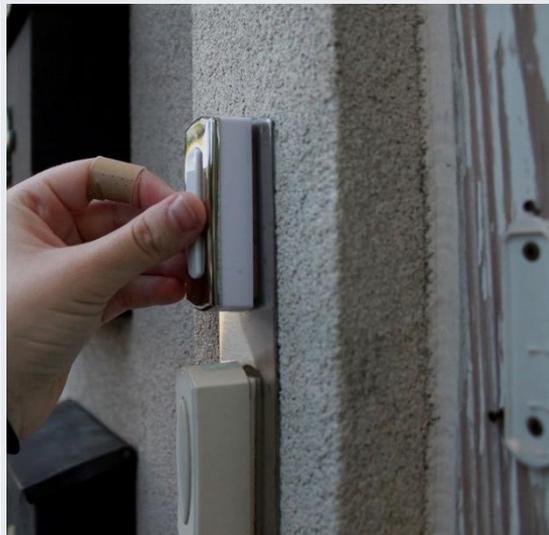
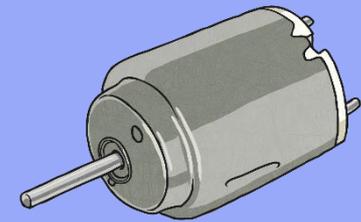
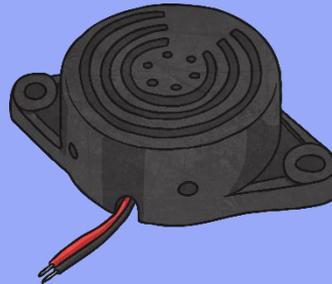
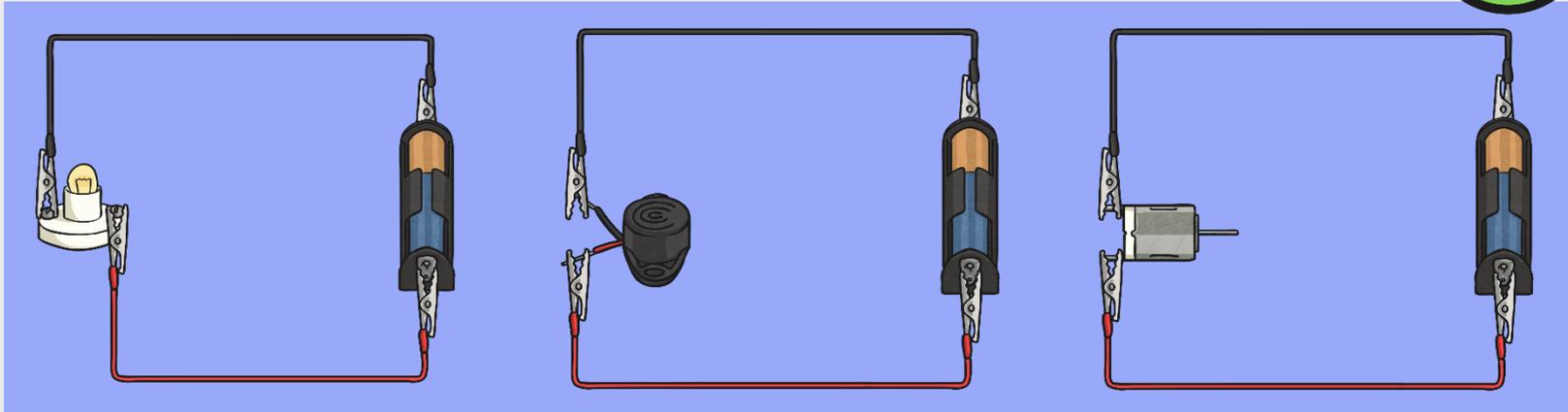
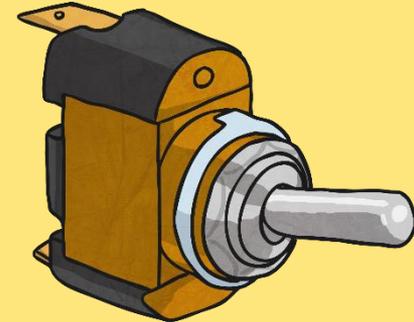


Photo courtesy of Paragon Apartments and alexa fades away (@flickr.com) and Greg Hume @Wikimedia Commons - granted under creative commons licence - attribution

Complete Circuits

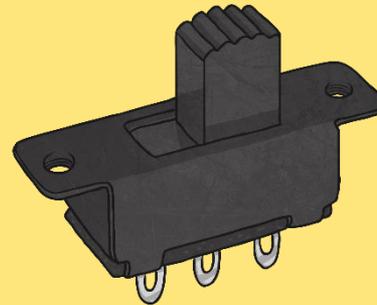








Switches!

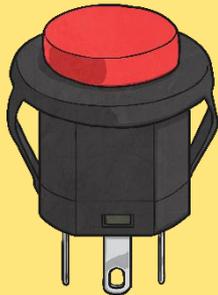

Switches



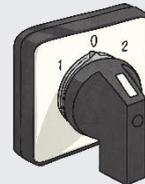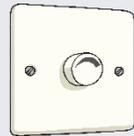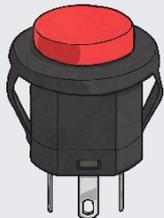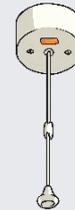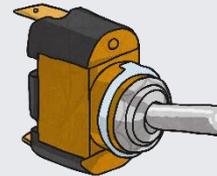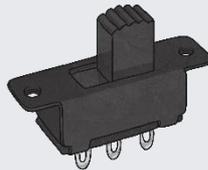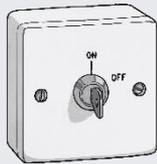There are a wide variety of switches that can be used.
Match the type of switch and its name.



slide switch

push button switch

pull switch

dimmer switch

paddle switch


selector switch

key switch

toggle switch

How Switches Work


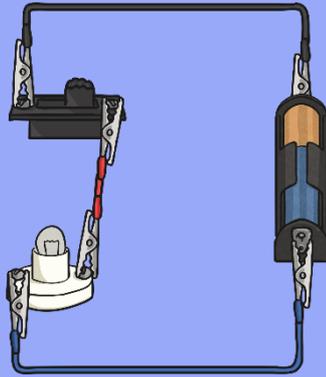
A **switch** 'breaks' a complete circuit on purpose to stop the flow of **electrons** when it is **off**.



When the **switch** is **on**, the circuit is complete and so the **electrons** are able to flow around the circuit.



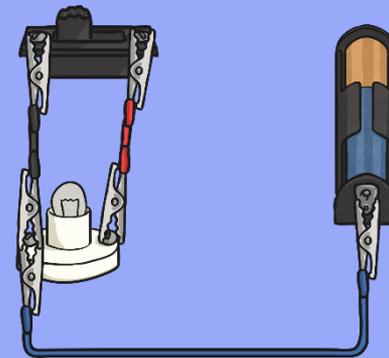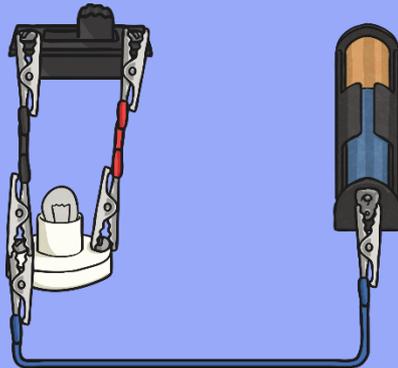A **circuit with a switch** is not the same as an **incomplete circuit**. In an **incomplete circuit**, the **electrons** are unable to flow at all **whether the switch is on or off**.



Aim



- I can explain how a switch works and why they are needed.

Success Criteria

- I can explain that a switch turns the electric current on and off.
- I can create a circuit containing a switch.

